



UNIVERSITY OF WASHINGTON

BEE331 LAB 4

<i>2301991</i>	<i>2130474</i>
<i>Jason Truong</i>	<i>Henry Haight</i>

supervised by
Prof. Joseph DECUIR

August 9, 2024

NMOS Amplifier Circuit

Design Objective

In this lab, we introduce ourselves to the MOSFET Amplifier. We characterise and build an audio-amplifier's small-signal single-stage circuit.

Circuit Design Outline

With a sinusoidal voltage source V_{AC} - @ $V_p = 50mV$ and a frequency of $10kHz$ in series with a capacitor $C_{C1} = 0.1\mu F$. In parallel - a series DC voltage source V_{DD} connected to a resistor $R_{G1} = 38.2k$, another resistor $R_{G2} = 95.3k$, and Gate to an NMOSFET $NMOS_G$.

From the NMOSFET,

- Source

Parallel, a capacitor $C_s = 10\mu F$ and resistor $R_S = 200\Omega$.

- Drain

In parallel - a resistor $R_D = 500\Omega$, to a series Capacitor C_{C2} and Resistor R_L .

Analysis

- **1.2.3 Calculate the Voltage gain of the amplifier circuit of Figure 6 using the following two equations:**

$$\frac{v_o}{v_{sig}} = g_m R_d$$

$$g_m = k_n V_{ov} = \frac{2I_D}{V_{ov}}$$

- **2.3 How does the calculated voltage gain (using $\frac{v_o}{v_{sig}} = g_m R_D$) compare with the measured voltage gain? Explain the potential sources of error. You can reference your explanation to the more precise expression for the voltage gain.**

How does the calculate Voltage Gain compare?

See addendum for calculations

Sources of Error

Imperfect Components

Imprecise Calculations (approximates)

Metrics of R_D leading to a lowered measured gain.

Measurements error overall.

- **2.4 Give a brief summary of how your audio amplifier worked and what gain in decibels ($|A_v|_{dB} = 20\log(\frac{v_o}{v_{sig}})$) you achieved at 10 kHz)**

[See addendum for calculations]

The audio amplifier's output is dependent on the ratio of $\frac{v_o}{v_{sig}}$.

- **2.5 How would you increase the gain by an additional 10 dB? How does the gain behave as a function of frequency?**

[See addendum for calculations]

Understand voltage gain in dB $20\log \approx 3.16$

$$A_v^{new} = 3.16 * A_v^{original}$$


Increasing the value of the Midband $g_m R_D$

Decreasing the High-Frequency Roll-Off in the MOSFET

Gain behaves as a function of frequency in relation to $v_{sig} = V_p \cos(2\pi f + \phi)$.

Figure 1: MOSFET Amplifier

(a) NMOS Amplifier

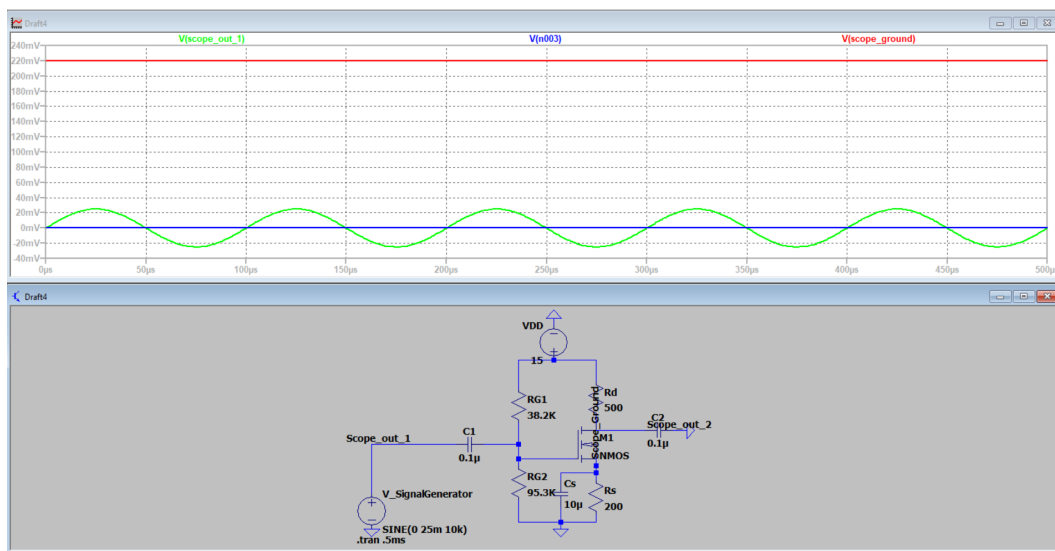


Summary & Conclusions

Revealed in Figure RD-Circuit 1A & 1B, the generated oscilloscope readings of the two periodic function match the characteristics of the transfer function found in 1b (RD Circuit). So the measurements do infact closely align.

Figure 2: Jason Truong Addendum

(a) Lab 4 Calculations

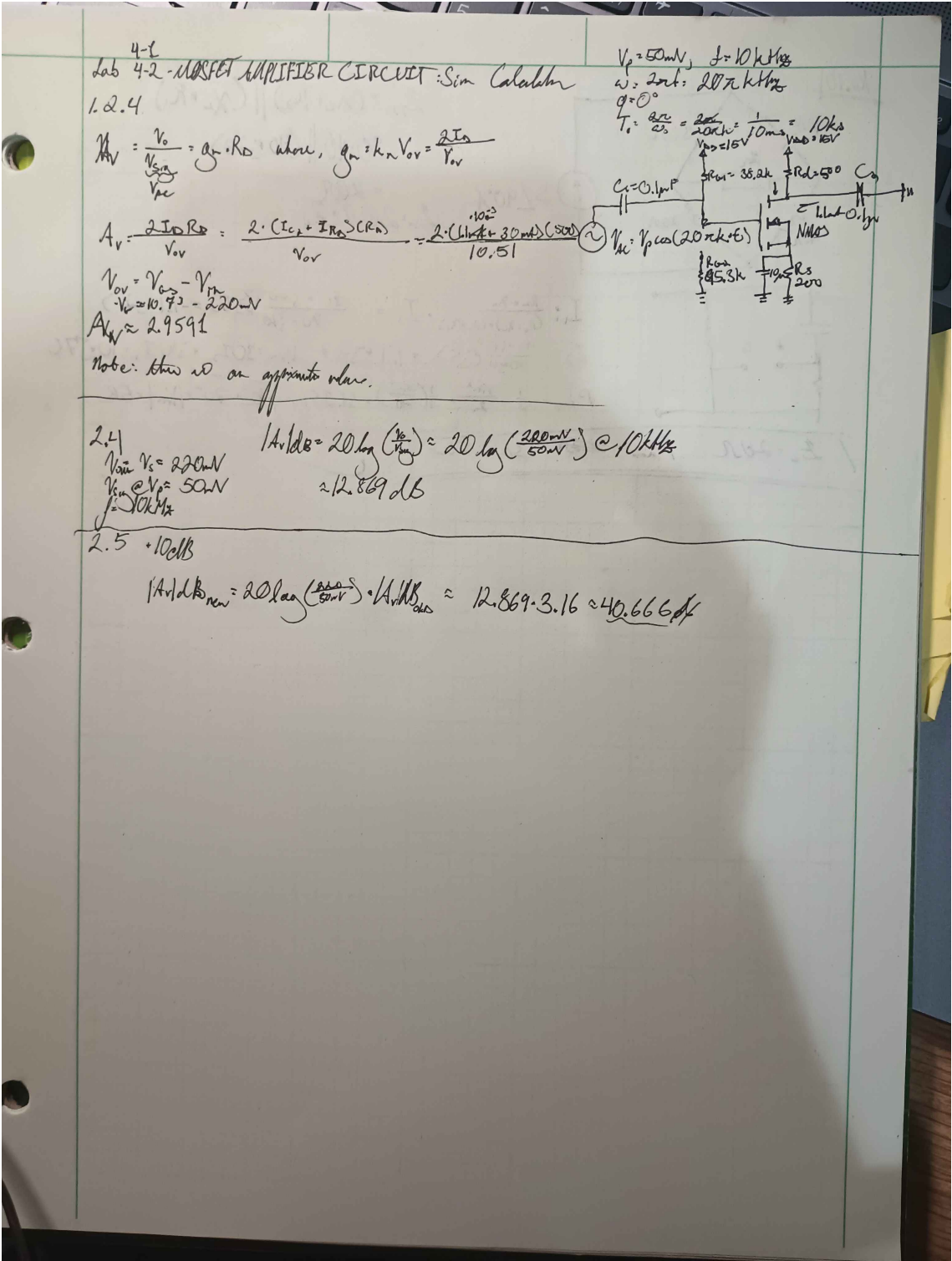

Bibliography
Cited:

- Lab 1 Manual
- Sedra, Adel, and Kenneth Smith. Microelectronic Circuits. S.L., Oxford Univ Press Us, 2019.
- "How Do You Calculate, a Silicon Junction Diode with N = 1 Has v = 0.7 v al I = 1 MA. What Is the Voltage Drop at

I=0.1 MA and I=10 MA.?” Quora, 2024, appliedmathematics.quora.com/How-to-calculate-A-silicon-junction-diode-with-n-1-has-v-0-7-V-at-I-1-mA-What-is-the-voltage-drop-at-I-0-1-mA-an?top_ans=223007030. Accessed 15 July 2024.



(a) Good work.